TK-1B WIGHT MILLIAMS MONOSCOPE CAMERA



RADIO CORPORATION OF AMERICA ENGINEERING PRODUCTS DEPARTMENT CAMDEN, N. J.

ROBERT M. WILSON INDUSTRY SERVICE ABORATORY SEr 4-1952

my hunch about RCAI worked. Here is a TK-18
Manual which you may
Keep

Bak

Jarry Williams
RCA Fols 1970

TK-1B MONOSCOPE CAMERA

ES-26960-A

INSTRUCTIONS

Copyright 1950

RADIO CORPORATION OF AMERICA

RCA Victor Division

Manufactured by

RADIO CORPORATION OF AMERICA

ENGINEERING PRODUCTS DEPARTMENT

Camden, New Jersey, U. S. A.


WARNING

THE VOLTAGES EMPLOYED IN THIS EQUIPMENT ARE SUFFICIENTLY HIGH TO ENDANGER HUMAN LIFE AND EVERY REASONABLE PRECAUTION HAS BEEN OBSERVED IN DESIGN TO SAFEGUARD THE OPERATING PERSONNEL. THE POWER SHOULD BE REMOVED COMPLETELY BEFORE CHANGING TUBES OR MAKING INTERNAL ADJUSTMENTS.

FIRST AID IN CASE OF ELECTRIC SHOCK

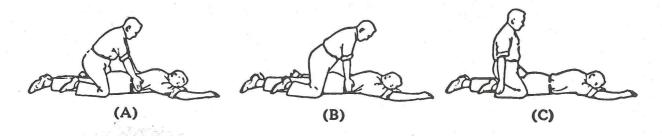- 1. PROTECT YOURSELF with dry insulating material.
- 2. BREAK THE CIRCUIT by opening the power switch or by pulling the victim free of the live conductor.

DON'T TOUCH VICTIM WITH YOUR BARE HANDS until the circuit is broken.



- 3. LAY PATIENT ON STOMACH, one arm extended, the other arm bent at elbow. Turn face outward resting on hand or forearm.
- 4. REMOVE FALSE TEETH, TOBACCO OR GUM from patient's mouth.
- 5. KNEEL STRADDLING PATIENT'S THIGHS. See (A).
- 6. PLACE PALMS OF YOUR HANDS ON PATIENT'S BACK with little fingers just touching the lowest ribs.
- 7. WITH ARMS STRAIGHT, SWING FORWARD gradually bringing the weight of your body to bear upon the patient. See (B).
- 8. SWING BACKWARD IMMEDIATELY to relieve the pressure. See (C).
- 9. AFTER TWO SECONDS, SWING FORWARD AGAIN. Repeat twelve to fifteen times per minute.
- 10. WHILE ARTIFICIAL RESPIRATION IS CONTINUED, HAVE SOMEONE ELSE:
 - (a) Loosen patient's clothing.
 - (b) Send for doctor.
 - (c) Keep patient warm.
- 11. IF PATIENT STOPS BREATHING, CONTINUE ARTIFICIAL RESPIRATION. Four hours or more may be required.
- 12. DO NOT GIVE LIQUIDS UNTIL PATIENT IS CONSCIOUS.

TABLE OF CONTENTS

| | | No. |
|---|----|-----|
| TECHNICAL SUMMARY | | 4 |
| Electrical Characteristics | ., | 4 |
| Tube Complement | | 4 |
| Mechanical Specifications | | 4 |
| EQUIPMENT | | 4 |
| DESCRIPTION | | |
| General | | 5 |
| Circuits | | 5 |
| INSTALLATION | | 8 |
| Installing Monoscope Tube | | 8 |
| Connecting Cables | | 8 |
| Initial Adjustments | | 9 |
| OPERATION | | 10 |
| Interpretation of Test Pattern | | 10 |
| MAINTENANCE | | |
| PARTS LIST | | 12 |
| | | 111 |
| | | |
| | | |
| LIST OF ILLUSTRATIONS | | |
| Figure No. | | |
| 1 Block Diagram, Monoscope Camera (P-728972, sub 1) | | 6 |
| 2 Fundamental Damper Circuit (K-893491, sub 0) | | 7 |
| 3 Horizontal Damper Circuit (M-445710, sub 1) | | 7 |
| 4 Picture Pattern, Monoscope Camera | | П |
| 5 Monoscope Camera, Front View — Panel Removed | | 16 |
| 6 Monoscope Camera, Rear View | | 17 |
| 7 Voltage and Waveform Chart | | 18 |
| 8 Schematic Diagram, Monoscope Camera (E-312332, sub 0) | | |

TECHNICAL SUMMARY

ELECTRICAL CHARACTERISTICS

| 0.5 5 100/ 1 |
|--|
| 3.5 to -5 volts, 10% hor. cycle |
| 3.5 to -5 volts, 4% vert. cycle |
| 3.5 to -5 volts, RMA std. |
| |
| 1.5 volts, max. |
| |
| 1.5 volts video plus 0.5 volt sync., or 2 volts composite, |
| |
| white in positive direction. Impedance 75 ohms. |
| |
| 3 volts (centering) and 300 ma at 280 volts |
| 110/120 volts, 50/60 cycles, 100 watts |
| dified by optional addition of blanking and synchro- |
| diffica by optional addition of bearing same |
| |
| |
| Type 6SN7GT 1 RCA Type 1B3GT/8016 |
| Type 6V6GT 1 RCA Type 2F21 |
| Type 6Y6G 1 RCA Type 991 |
| |
| |
| |
| |
| 19 inches |
| |
| |
| |

EQUIPMENT

The TK-1B Monoscope Camera is supplied as MI-26030-A and includes all tubes in place except the Monoscope tube. This tube, type 2F21, is shipped separately and carries the RCA reference number MI-26657. A square set of tubes may be ordered as MI-26679-A.

For necessary interconnections one 10-prong Jones plug, five coaxial connectors, and six 75-ohm coaxial terminations are supplied with the equipment. Cable required but not supplied is as follows:

- 1 Five-wire cable from the d-c power supply—2 wires for a-c connection, 2 wires for d-c voltage, and 1 wire for centering voltage.
- 1 Interconnecting cable for remote focus and gain controls (if used).
- Required number and length of 75-ohm cables for installation.

A d-c power source such as from the RCA Type 580-C Regulated Power Supply, MI-21523-B1, is required for the Monoscope Camera. Synchronizing pulses may be obtained from the RCA Type TG-1A generator, MI-26915.

DESCRIPTION

GENERAL

The Type TK-1B Monoscope Camera has been designed to produce a video signal of high and dependable quality for use with or without synchronizing pulses. The fixed pattern provided is suitable for checking resolution capabilities, low-frequency phase shift, contrast, and deflection linearity of other television studio equipment, as well as providing a modulating signal for transmitters. When the camera output is employed to modulate an r-f signal generator, the resultant signal may be used to check receiver performance. The Monoscope Camera utilizes a recessed type chassis designed for mounting in a standard 19-inch rack or cabinet.

Four paralleled connectors make it possible to feed the input signals through to other equipment without disturbing the camera circuits. Three other coaxial connectors provide for the camera output, and seven pin jacks on the chassis enable a rapid check to be made on all input and output signals.

A narrow panel near the lower part of the unit contains the eight most important operating controls while the chassis mounts five screwdriver adjustments. An interlock circuit removes all high voltage when the front panel is removed. A shorting plug clipped to the panel enables the interlock to be bypassed when required during servicing or test.

Low-plate voltage for the Monoscope Camera requires a source of 280 volts d-c at 300 ma; the high-voltage circuit in the camera requires 110/120 volts a-c, 50/60 cycles. A 10-prong Jones plug on the chassis provides for connecting these two circuits.

CIRCUITS

Monoscope Tube

The basic operation of the Monoscope Camera is illustrated on the block diagram, Figure 1. Source of the picture signal is the Monoscope tube which contains a fixed pattern of carbon deposited on an aluminum plate. Advantage is taken of the different secondary emission characteristics of the aluminum and carbon pattern.

When the fixed pattern is scanned, electrons emitted are collected on an electrode which is in the form of a conductive coating on the tube. Although this coating is a-c coupled to ground, it is at a positive potential with respect to the pattern. The picture signal, therefore, appears between the pattern plate and ground.

The high voltage circuit in the unit supplies the accelerating and focusing potentials for the scanning beam. Deflection of the beam is achieved magnetically by horizontal and vertical deflection yokes which fit over the neck of the tube. Sawtooth scanning currents are supplied to the yokes by horizontal and vertical deflection circuits in the unit. Driving pulses for the deflection circuits must be furnished by an external synchronizing generator.

Vertical Deflection Circuit

As shown on the overall schematic diagram, Figure 8, vertical driving pulses from the synchronizing generator are inserted at either of the two paralleled connectors, J7 or J8. Amplification of the driving pulses is obtained in one triode section of V14, while the second section is utilized as a sawtooth generator. "Height" is controlled by potentiometer R96 in the plate circuit of V14.

Both sections of sawtooth amplifier V13 are connected in cascade to increase the voltage to the proper vertical driving level for the output tube V12A. Transformer T2 couples V12A to deflection coil L8.

The grid and cathode of vertical feedback amplifier V11A are connected across R109 which is in series with the vertical deflection coil L8. Resistor R109 also connects to the center tap on VERT. CENT. potentiometer R131. Control R131 is part of the grid leak circuit of V11A and has effect over the entire raster.

Horizontal Deflection Circuit

Horizontal driving pulses are fed into either J9 or J10. These connectors are coupled to one section of V18 which is utilized as a horizontal driving pulse amplifier. The other section of V18 is used as a sawtooth generator, "width" being controlled by R116.

Output from V18 is fed through V17, and through T3 to the horizontal deflection coils L7 and damper tube V16. Tube V16 provides control of horizontal deflection linearity and maximum utilization of available power. Figure 2 illustrates the fundemental damper circuit while

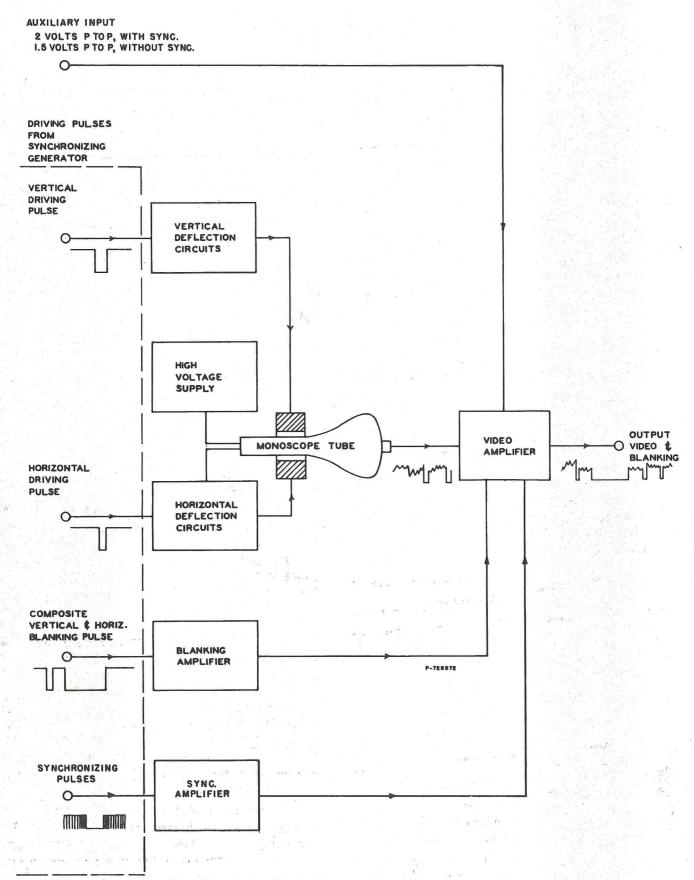


Figure 1-Block Diagram, Monoscope Camera

Figure 3 is an extraction from the overall schematic diagram. Potentiometers R127 and R126 are the HOR LIN A and HOR LIN B controls, respectively.

Blanking Amplifier

Blanking pulses through J5 or J6 are amplified by V9B and V7. By connecting the plate of V7 directly to the plate circuit of V2, the amplified blanking pulses are coupled to the video amplifier stages.

Video Amplifier

The seven-stage video amplifier, V1 to V8, is of the series-shunt peaked type. To compensate for the distributed capacity at the Monoscope output, a high-peaking circuit is added between V5 and V6. Frequency response of the other stages is essentially flat to 8 mc. The two output stages, V8 and V10, are identical.

GAIN control, R36, is connected into the screen grid circuit of V2 while R83, BRIGHT-NESS control, functions to control black level in a linear clipper circuit. The "Transient Suppressor," R44, is set at about 1.5 volts above the screen voltage on V3.

The auxiliary signal input, J1 or J2, permits the optional mixing of special test signals with blanking and synchronizing pulses. Thus signals such as from a sweep generator or grating generator may be passed through a unity gain amplifier, V2 and V3. Blanking is added in the common plate load of V2 and V7, while optional synchro-

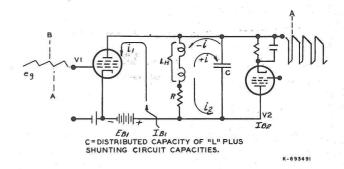


Figure 2-Fundamental Damper Circuit

nizing pulses are added at the screen grid of V3. After mixing, the test signal then contains the necessary requisites for transmitter modulation. The AUX IN toggle switch, S1, on the chassis provides control of this circuit.

Synchronizing Amplifier

Synchronizing pulse inputs at J3 or J4 are passed through two amplifying stages, V9A and V12B, before insertion in the screen grid circuit of V3. Control of these pulses is provided by SYNC GAIN potentiometer R66, in the cathode circuit of V9A.

H. V. Power Supply

High voltage for the Monoscope tube, V20, is obtained from a power supply in the unit. Transformer T1 supplies heater voltages for all tubes as well as the high voltage for V20. An

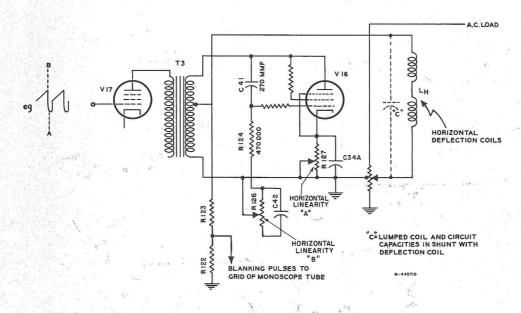


Figure 3—Horizontal Damper Circuit

1B3GT/8016 tube, V15, serves as the high-voltage, half-wave rectifier.

The positive side of the high-voltage is grounded so the signal plate of the Monoscope will be at ground potential. FOCUS control R80 and BRIGHTNESS control R83 are part of the output bleeder which supplies the required Monoscope voltages.

Negative bias for the clipping action in V3 is also supplied by V15, while V11B serves as a voltage regulator. Fuse F1 and interlock S2 are connected in the primary circuit of T1.

Remote Operating Circuits

For remote focusing of the Monoscope tube,

a 2.5 megohm potentiometer may be connected to pin 6 of J15 as shown on Figure 8. This control may be utilized if the picture monitor is located at a distance from the Monoscope Camera.

Similarly, a 100,000-ohm potentiometer connected between pin 5 of J15 and ground may be utilized as a remote gain control.

Miscellaneous

Pins 10 and 12 of J15 are utilized for connecting the external d-c 280-volt supply required for low plate and screen voltages. The -3 volts centering potential is connected to pin 11, while pins 7 and 8 of J15 require 110/120, 50/60 cycle ac power connections.

INSTALLATION

After unpacking, check the unit for damage incurred during shipment. Then remove the front panel and inspect all tubes to insure that they are firmly seated in their sockets.

Next, mount the unit in the rack or cabinet. Mounting screws are not supplied.

INSTALLING MONOSCOPE TUBE

To install the Monoscope tube, swing the hinged metal tube shield away from the chassis. Remove the top shield cover.

Insert the tube in the shield, rotating the tube so that the collector pin is accessible through the hole in the shield. Tighten the clamp on the lower end of the shield, to hold the tube in position.

Connect the red lead to the collector pin on the side of the tube.

Connect the black lead to the plate pin on the face of the tube. Position the wire so that it fits in the slot on the rim of the shield. Disconnecting the other end of this lead temporarily may facilitate making the connection. Be sure to reconnect it if removed.

Next replace the tube shield cover and swing the assembly back into place until locked by the pin and plug arrangement on the shield and chassis.

Attach the socket to the tube base, completing installation of this tube. Figure 5, the top chassis view, illustrates correct positioning of the leads to the tube.

CONNECTING CABLES

Two input taps are provided on the primary of transformer T1. If the measured line voltage ranges from 115 to 125 volts, the primary connec-

tion need not be changed since this is the asshipped condition. If the line voltage falls within the 105 to 115 volt limits, the black wire with red tracer should be disconnected from the fuse receptacle and the black lead with yellow tracer connected in its place. Tape the end of the lead removed.

Connect a suitable cable to the Jones plug in socket J15. The connections to be made are as follows:

| JACK J15 CIRCUIT | |
|--------------------------------------|-----|
| Pin 7,8 110/120 volt, 50/60 cycle ac | |
| Pin 10 280 volts dc, 300 ma, regular | ted |
| Pin 11 –3 volts dc | |
| Pin 12 Ground | |
| Pin 5 Remote gain (if required) | |
| Pin 6 Remote focus (if required) | |

Since no a-c switch is contained in the Monoscope Camera, it is advisable to parallel the camera supply with the a-c source to the low voltage power supply which may be an RCA Type 580-C unit. In this manner the power supply switch will control the a-c to the camera, insuring that the deflection circuits will be operating while high voltage is on the Monoscope tube. This arrangement aids in preventing possible damage to the Monoscope tube.

Connect the driving, blanking, synchronizing pulse, and output cables as indicated adjacent to the seven coaxial jacks. Since an unterminated line causes reflections which may alter the shape of an incoming signal, use should be made of the 75-ohm line terminations supplied. These terminations plug into the auxiliary input connectors

and should be used when a cable is not terminated or not "looped" through to other equipment.

When used, connect a monitor to the MONITOR OUTPUT jack. Insertion or removal of the monitor plug will not affect the camera's signal output.

INITIAL ADJUSTMENTS

Several initial adjustments must be made on the Monoscope Camera before routine operation. Since some of the controls are located on the chassis, the front panel must be removed during the following procedure, and the interlock shortcircuited.

First, remove the interlock shorting plug from the front panel clips and place it in the interlock receptacle.

Set both remote controls, if used, at the midposition.

Set the Monoscope GAIN control at midrange.

Turn BEAM control counterlockwise to minimum.

Energize the low-voltage power supply and allow one minute for the equipment to warm up.

Make certain both vertical and horizontal driving pulses are present at the camera input jacks.

DANGER

AT ALL TIMES KEEP HANDS AWAY FROM THE PLATE LEAD OF THE HIGH-VOLTAGE RECTIFIER TUBE, V15. THIS LEAD IS AT A POTENTIAL OF 1250 VOLTS WITH RESPECT TO GROUND.

Using the monitor oscilloscope as an indicator, set the blanking voltage to the desired amplitude by means of the BRIGHTNESS control. Adjust the raster in the monitor kinescope for the standard 4-to-3 aspect ratio.

Turn up the BEAM control until a picture appears on the monitor kinescope.

If the picture is rotated with respect to the raster, it may be aligned by loosening the two thumbscrews which hold the yoke against the Monoscope tube shield, and rotating the yoke.

Adjust for best focus with FOCUS control.

Adjust WIDTH, HEIGHT, VERT. CENT., and HOR. CENT. controls so that the picture in the monitor kinescope completely fills the raster.

Controls R126 and R127 are horizontal deflection linearity adjustments. H. LIN. A control, R127, should be set in the vicinity of from one-half to three-quarters maximum clockwise rotation. H. LIN. B control, R126, adjusts the scanning distribution on the righthand side of the picture. By careful adjustment of these controls a high degree of horizontal linearity can be achieved. Variable resistance R108, V. LIN., controls the vertical scanning linearity. These three screwdriver controls are mounted on the chassis and are indicated on Figure 5.

Synchronizing pulse height is controlled by SYNC. GAIN control R66, while R83, BRIGHT-NESS control, enables the black level to be adjusted. These two screwdriver controls are also pointed out on Figure 5. If necessary to adjust the TRANSIENT SUPP. potentiometer, measure the voltage from the control arm to ground and set it for a potential approximately 1.5 volts above the screen voltage on V3.

Deflection linearity may be checked by measuring the spacing between the horizontal and vertical cross lines in the Monoscope pattern, Figure 4. The dashed lines in each wedge also serve as the center lines in this cross line pattern.

Linearity may be established independently of the viewing monitor by use of a grating generator such as the RCA Type WA-3A unit. The grating generator signal is simply connected to the AUX IN jack on the camera. Then, to mix the generator signal with the Monoscope pattern, temporarily disconnect the lead from the contact on S1 to ground and connect it to pin 3 or 5 of the socket for V2. Switch S1 should remain in the OFF position for this operation. After the linearity adjustment the lead should be reconnected to ground.

Using the monitor oscilloscope as an indicator, the blackest part of the picture signal should now be brought down to the blanking level. It is well to keep the beam intensity as high as possible in order to achieve the maximum signal-to-noise ratio in the video amplifier. Care should be taken however not to use too high a beam intensity since this causes enlargement of the beam with consequent loss in resolution.

After making all necessary adjustments, the auxiliary interlock plug should be removed from the receptacle and replaced in its holder on the front panel. Secure the front panel to the chassis.

OPERATION

To operate the Monoscope Camera throw the power switch on the low voltage rectifier unit to the "ON" position. After the required warm-up period it may be necessary to make some slight readjustments of the gain, focus, and scanning controls. These panel controls will have to be readjusted from time to time as the tubes age.

INTERPRETATION OF TEST PATTERN

In Figure 4, the test pattern of the RCA type 2F21 Monoscope tube is illustrated. The outside diameter of the large circle is three-fourths the pattern width. Therefore, when the deflection is adjusted so as to give a true, or undistorted form to this circle, the standard aspect ratio of 4-3 is established.

The five sets of vertical and horizontal resolution wedges are calibrated in number of lines resolution, i.e. the numbers indicate the total number of alternate black and white lines of equal width which can be contained in the height of the picture. Resolution lines are of equal width in both horizontal and vertical directions. Hence, the total number of lines which can be contained in the width of the picture is greater than the number contained in the height by a factor equal to the aspect ratio (1.33).

The dashed center line of each wedge indicates the calibration point of the value adjacent to it. The calibrations 20, 30, etc., multiplied by 10

indicate the number of lines resolution. The point on the vertical wedges where distinction between individual lines just disappears, indicates the horizontal resolution of the system or equipment under test.

In the case of the horizontal wedges, vertical resolution is indicated by the calibration of the point where separation between lines just becomes indistinguishable. The principal set of wedges in the central part of the pattern, as well as those in each of the four corners, provides an indication of the quality focus. This applies especially to the corner wedges where defocusing is most likely to prevail.

The diagonal wedges simulate a density range extending from black towards white. With the brightness adjusted so that the innermost portion is black, or 100 percent, the remaining three sections of each wedge are respectively 75, 50, and 25 per cent of black.

Thin line grids extending over the pattern provide an additional check on the horizontal and vertical deflection linearity. The diagonal bars indicate the boundaries of a section which is one-half the overall pattern width. The horizontal bars beneath the small circle vary logarithmically in length. The amount of streaking following the end of the bar in the change from black to white, indicates the quality of the low-frequency response of the circuits under test.

MAINTENANCE

WARNING

HIGH VOLTAGES INJURIOUS TO LIFE ARE PRESENT IN THE UNIT. USE GREAT CARE IN MEASURING TUBE VOLTAGES. HEAVY, WELL-INSULATED TEST PROBES SHOULD BE USED IN CONJUNCTION WITH A METER CAPABLE OF MEASURING AT LEAST 1500 VOLTS.

Little attention is required to keep the Monoscope Camera in good working condition. Periodic inspections should be started dating from the time the unit is placed in operation. These inspection periods should be no longer than thirty days apart. During these inspections the unit should be cleaned and dusted thoroughly. All tubes should be checked. Any tube showing weak or sluggish emission should be replaced with a tube known to be good.

In the event faulty operation does occur, a

typical voltage and waveform chart is supplied on Figure 7. When measuring tube voltages any measurement plus or minus twenty per cent of the typical voltage readings is an indication of a fault in the circuit being measured.

The high voltage supply has a 1.5 ampere fuse, F1, in series with one side of the power source. Under no circumstance replace this fuse with one having a higher current rating. In the event a replaced fuse burns out, ascertain and clear the fault in the unit before inserting another.

Seven chassis pin jacks, labeled BLANK, AUX, PIX, V. DRIVE, SYNC, H. DRIVE, and MON., enable these circuits to be tested rapidly from the front of the unit. In addition these test jacks make it unnecessary for any external cables to be removed. Symbol numbers of the jacks are J2, 12, 14, 16, 17, 18, and 20.

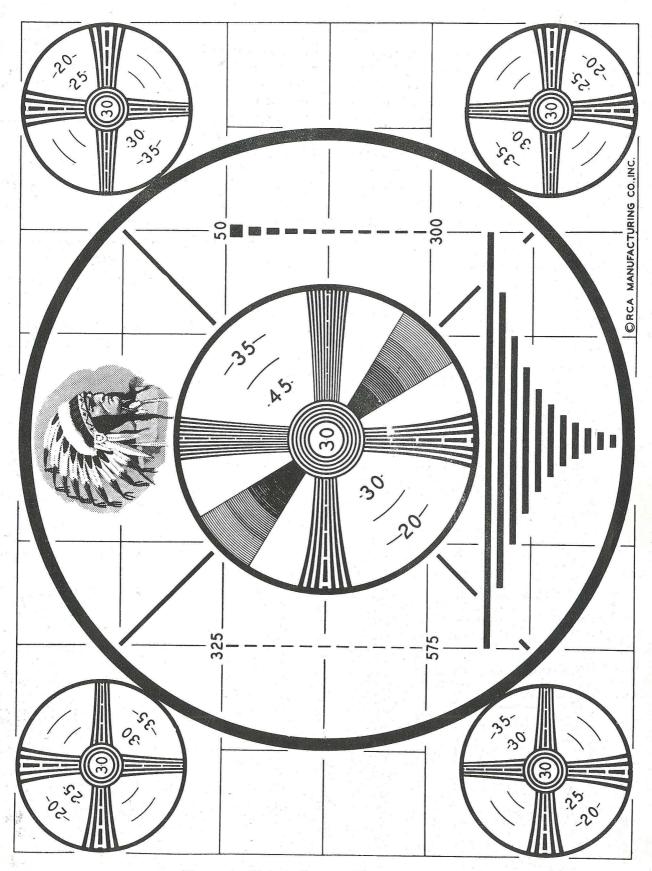


Figure 4-Picture Pattern, Monoscope Camera

PARTS LIST

When ordering replacement parts, please give RCA Stock Number. Symbol Number, Description, and Drawing Number will be helpful in further identifying the desired part and should be given when no Stock Number is shown in the following list.

The part which will be supplied against an order for a replacement, item may not be an exact duplicate of the original part, however, it will be

a satisfactory replacement, differing only in minor mechanical or electrical characteristics. Such differences will in no way impair the operation of the equipment.

Symbol Numbers with suffix letters may not be shown on the schematic. They are used for relating the parts to the main item of which they are components.

MONOSCOPE CAMERA

| SYMBOL No. | DESCRIPTION | DRAWING No. | STOCK No. |
|------------------------------------|--|---------------------------------------|---------------------|
| C1 C2 C2A/B | Capacitor, 0.25 mf, 600 volts Capacitor, 1000-1000 mf, 15 volts Capacitor, part of C2 | K-8887706-12 B-442900-40 | 59751 59757 |
| C3 C3A/B | Capacitor, 80-10 mf, 400 volts | M-442900-33 | 59758 |
| C4 C5 | Capacitor, 0.047 mf, 400 volts | C-735715-171 | 73553 |
| C6 C7 C7A/B/C and D | Capacitor, same as C4 Capacitor, 20-10-10 mf, 450 volts Capacitor, part of C7 | B-442900-30 | 59759 |
| C8 C9 | Capacitor, same as C4 Capacitor, variable, 7-45 mmf | K-868903-3 | 54221 |
| C10 C10A/B C11 | Capacitor, same as C3 Capacitor, part of C10 Capacitor, same as C4 | * * : : : * | |
| C12, C13 C14 C15 | Capacitor, 330 mmf, 500 volts. Capacitor, 0.47 mf, 400 volts. Capacitor, same as C12 | P-727851-135 C-737818-96 | 59484 59512 |
| C16 C16A/B | Capacitor, 20-20 mf. 450 volts | M-95695-39 | 34889 |
| C17 C18 | Capacitor, part of C16 Capacitor, same as C14 Capacitor, same as C16 Capacitor, 1 mf, 600 volts | 77 0000000 | |
| C19, C20 C21 C22 C22A/B | Capacitor, 0.22 mt, 400 volts | K-8887706-14 C-735718-179 | 45807 74957 |
| C23 C24 C25 | Capacitor, same as C3 Capacitor, part of C22 Capacitor, same as C21 Capacitor, same as C16 Capacitor, 8200 mmf, 1600 volts | C-735715-462 | 73821 |
| C26 C27 C28 | Capacitor, 1 mf, 1500 volts Capacitor, 2 mf, 1000 volts Capacitor, same as C26 | K-984629-123 K-984629-113 | 58481 59760 |
| C29, C30, C31 C32, C33 | Capacitor, 0.1 mf, 600 volts Capacitor, same as C21 | C-735715-275 | 73557 |
| C34, C33 C34 C34A/B C35 | Capacitor, 0.5-0.5 mf, 400 volts Capacitor, part of C34 Capacitor, game as C30 | K-984680-417 | 56913 |
| C36, C37 C38 C39 | Capacitor, 0.01 mf, 600 volts Capacitor, 270 mmf, 500 volts Capacitor, same as C36 | C-735715-263 P-727851-133 | 73565 59483 |
| C40 C40A/B | Capacitor, same as C34 Capacitor, part of C40 | | 1.0 |
| C41 C42 C43 C44 | Capacitor, same as C38 Capacitor, same as C36 Capacitor, same as C29 Capacitor, same as C29 | | , J |
| C44 F1 J1 J2 J3 to J11 | Capacitor, same as C29 Capacitor, same as C12 Fuse, 1.5 amperes Connector, jack Jack, tip Connector, same as J1 | K-55544-2 P-255223-1 K-845648-1 | 272 5180 1834 |
| T12 T13 T14 | Iack, same as J1 Connector, same as J1 Jack, same as J2 | | |
| J15 | Connector | P-727969-11 | 51928 |

| SYMBOL No. | DESCRIPTION | DRAWING No. | STOCK No. |
|-------------------|--|-----------------------------|----------------|
| J16, J17, J18 | Jack, same as J2 | | |
| J19 | Connector, receptacle | M-445813-4 | 54890 |
| J20 L1 | Jack, samé as J2 Coil | P-739772-505 | 51906 |
| L1A/B | Coil, part of L1 | | |
| L2 L2A/B | Coil, same as L1 Coil, part of L2 | | |
| L3 | Coil, part of L2 Coil Coil, part of L3 | P-739772-506 | 51907 |
| L3A/B L4 | Coil, same as L3 | | |
| L4A/B L5 | Coil, part of L4 Coil, same as L3 | 2 | |
| L5A/B | Coil part of L5 | | #4000 |
| L6 | Coil, reactor Coil, assembly | M-901919-1 K-8883411-501 | 51909 54604 |
| L7 L8 | Coil. deflecting voke | P-727966-501 | 51913 |
| P1 | Connector, plug | K-252868-1 | 66344 |
| P2 P3 | Not Used Connector, same as P1 | | 2 2 |
| P4 | Not Used | | |
| P5 P6 | Connector, same as P1 Not Used | | |
| P7 | Connector, same as P1 | | |
| P8 P9 | Not Used Connector, same as P1 | | |
| P10 to P14 | Not Used | 7 | |
| P15 P16 to P18 | Connector, plug Not Used | P-727969-12 | 51929 |
| P10 to F16 | Connector, UG-260/U | M-427992-501 | 56153 |
| R1 | Resistor, 100,000 ohms, 1 watt | K-90496-86 K-82283-86 | 7263 325 |
| R2 R3 | Resistor, 100,000 ohms, ½ watt. Resistor, 100 ohms, ½ watt. | K-82283-50 | 3476 |
| R4 | Resistor, 150 ohms, ½ watt | K-82283-52 K-90496-83 | 30880 17440 |
| R5 R6 | Resistor, 56,000 ohms, 1 watt Resistor, same as R3 | K-90490-65 | 1/440 |
| R7 | Resistor, 10,000 ohms, 1/2 watt. | K-82283-74 | 3078 |
| R8 R9 | Resistor, 1500 ohms, ½ watt | K-82283-64 K-90496-74 | 30654 71914 |
| R10 | Resistor, 470,000 ohms, ½ watt | K-82283-94 | 3064 |
| R11 R12 | Resistor, same as R3 Resistor, same as R4 | | |
| R13 | Resistor same as R5 | | 10/10/05 |
| R14 R15 | Resistor, 6800 ohms, 1/2 watt | K-82283-72 | 14659 |
| R16 | Resistor, 220 ohms, 1 watt | K-90496-54 | 3904 |
| R17 R18 | Resistor, same as R10 Resistor, same as R3 | | a 'a el |
| R19 | Resistor, 82 ohms, ½ watt | K-82283-49 | 1396 |
| R20 | Resistor, 18,000 ohms, 1 watt | K-90496-77 K-90496-59 | 1875 3888 |
| R21 R22 | Resistor, 120,000 ohms, 1 watt | K-90496-87 | 7263 |
| R23 | Resistor, 680 ohms, ½ watt | K-82283-60 | 1226 |
| R24 R25 | Resistor, same as R5 | | |
| R26 | Resistor, 5600 ohms, ½ watt | K-82283-71 | 3073 |
| R27 R28 | Resistor, 1200 ohms, ½ watt Resistor, 5600 ohms, 1 watt | K-82283-63 K-90496-71 | 3073 3888 |
| R29 | Resistor, same as R10 | | |
| R30 R31 | Resistor, same as R3 Resistor, 47 ohms, 1 watt | K-90496-46 | 4588 |
| R32 | Resistor, 33 ohms, ½ watt | K-82283-44 | 3078 |
| R33 R34 | Resistor, 220 ohms, ½ watt Resistor, same as R5 | K-82283-54 | 520 |
| R35 | Resistor, same as R1 | | - 2 |
| R36 R37 | Resistor, variable, 100,000 ohms Resistor, 2200 ohms, ½ watt | M-433196-4 K-82283-66 | 5192 3476 |
| R38 | Resistor, 910 ohms $\pm 5\%$, 1 watt | K-90496-158 | 5976 |
| R39 R40 | Resistor, 470,000 ohms, 1 watt | K-90496-94 | 7252 |
| R40 R41 | Resistor, same as R3 Resistor, same as R4 | | |
| R42 | Resistor, 33,000 ohms, 1 watt | K-90496-80 | 3889 |
| R43 R44 | Resistor, 10,000 ohms, 2 watts Resistor, variable, 5000 ohms | K-99126-74 M-433196-18 | 4429 5200 |
| R45 R46 | Resistor, 15,000 ohms, 2 watts Resistor, 8200 ohms, ½ watt | K-99126-76 K-82283-73 | 6893 1425 |

| R83 Resistor, 180,000 ohms, 1 watt | No. | DESCRIPTION | DRAWING No. | STOCK No. | |
|--|---------------|---|--------------------------------|----------------|--|
| Resistor, 560,000 ohms, 2 watt. Resistor, 580,000 ohms, 2 watt. Resistor, 580 ohms, 2 watts Resistor, 580 ohms, 2 watt Resistor, 580 ohms, 2 wat | | Resistor, 560 ohms, ½ watt | K-82283-59 | 516 | |
| RS2 | | Resistor, 27,000 onms, 2 watts | | 4421 | |
| R51 | | Resistor, 500,000 onms, ½ watt | | 3065 | |
| R52 Resistor, same as R3 R53 Resistor, 18,000 ohms, 2 watts K-99126-77 R54 Resistor, 18,000 ohms, 2 watts K-99126-77 R54 Resistor, and as R2 R55 Resistor, same as R4 R57 Resistor, same as R4 R58 Resistor, same as R4 R59 Resistor, 47 ohms, ½ watt R59 R61 | | | - cath , a State way | | |
| R531 Resistor, 18,000 ohms, 2 watts R54 Resistor, non-inductive, 3000 ohms, 5 watts R55 Resistor, same as R2 R56 Resistor, same as R2 R57 Resistor, same as R4 R58 Resistor, 1000 ohms, 1 watt R59 Resistor, 1000 ohms, 1 watt R59 Resistor, 500,000 ohms, 1 watt R59 Resistor, 500,000 ohms, 1 watt R50 Resistor, 47,000 ohms, 1 watt R52 R62 R63 R63 R64 R61 R63 R64 R65 | | Resistor, same as R3 | | | |
| Resistor, same as R40 Resistor, same as R42 Resistor, same as R44 Resistor, same as R49 Resistor, same as R54 Resistor, same as R56 Resistor, same as R57 Resistor, same as R68 Resi | | Resistor, 18,000 ohms, 2 watts | K-00126-77 | 3915 | |
| R55 Resistor, same as R49 R57 Resistor, 10 ohms, 1 watt R58 Resistor, 100 ohms, 1 watt R59 Resistor, 100 ohms, 1 watt R59 Resistor, 500,000 ohms, 1 watt R59 Resistor, 500,000 ohms, 1 watt R59 Resistor, 47,000 ohms, 1 watt R50 Resistor, 47,000 ohms, 1 watt R50 Resistor, 47,000 ohms, 1 watt R51 Resistor, 47,000 ohms, 1 watt R52 Resistor, 47,000 ohms, 1 watt R52 Resistor, 47,000 ohms, 1 watt R53 Resistor, 180 ohms, 1 watt R54 Resistor, 180 ohms, 1 watt R55 R65 Resistor, 180 ohms, 1 watt R56 Resistor, 180 ohms, 1 watt R57 Resistor, 470 ohms, 1 watt R57 Resistor, 470 ohms, 1 watt R58 R58 R59 | | Resistor, non-inductive, 3000 ohms, 5 watts | | 5162 | |
| R55 Resistor, 10 ohms, ½ watt | | Resistor, same as R2 | 112 110000 111 | 3102 | |
| Resistor, same as Resistor, resistor, law resistor, same as Resistor, resistor, law resistor, law resistor, law resistor, resistor, law resistor, resistor, law resistor, resistor, law resistor, resistor, resistor, law resistor, resistor | 2007 70 70 70 | Resistor, same as R49 | | | |
| Resistor, 360, 68 Resistor, 370, 600 Resistor, 360, 68 Resistor, 360, 68 Resistor, 370, 600 Resistor, 360, 68 Resistor, 360, 68 Resistor, 360, 68 Resistor, 360, 68 Resistor, 360 Resist | | Resistor, 10 000 ohms 1 watt | | 3476 | |
| R60 Resistor, 560,000 ohms, 1 watt K.90496-95 R61 Resistor, 47 ohms, ½ watt K.82283-46 R62 Resistor, 47 ohms, ½ watt K.82283-46 R63 Resistor, same as R1 K.90496-82 R64 Resistor, same as R4 K.90496-82 R65 Resistor, same as R4 K.82283-53 R66 Resistor, variable, 500 ohms. C.737829-5 R67 Resistor, same as R1 K.82283-87 R68 Resistor, same as R1 K.82283-97 R70 Resistor, same as R19 K.82283-97 R71 Resistor, same as R19 K.82283-97 R72 Resistor, same as R19 K.82283-97 R73 Resistor, same as R2 K.82283-84 R74 Resistor, same as R2 K.82283-84 R75 Resistor, same as R2 K.90496-92 R76 Resistor, variable, 50,000 ohms M.433196-5 R77 Resistor, same as R2 K.90496-92 R78 Resistor, same as R2 K.90496-89 R81 Resistor, same as R36 K.90496-89 </td <td></td> <td>Resistor, same as R42</td> <td>K-90496-62</td> <td>7191</td> | | Resistor, same as R42 | K-90496-62 | 7191 | |
| Resistor, 47 000ms, 1 watt. Resistor, 27 00ms, 1 watt. Resistor, same as R49 Resistor, same as R49 R66 Resistor, 180 olms, ½ watt R67 Resistor, 180 olms, ½ watt R68 Resistor, 180 olms, ½ watt R68 Resistor, 1 megohm, ½ watt R69 Resistor, 1 megohm, ½ watt R69 Resistor, same as R19 R70 Resistor, same as R19 R71 Resistor, same as R19 R72 Resistor, same as R19 R73 Resistor, same as R19 R74 Resistor, variable, 500,000 ohms, 1 watt R75 Resistor, variable, 500 ohms, 1 watt R76 Resistor, variable, 500 ohms, 1 watt R77 Resistor, same as R2 R78 Resistor, 1 megohm, 1 watt R79 Resistor, same as R2 R79 Resistor, 1 megohm, 1 watt R79 Resistor, same as R2 R79 Resistor, same as R3 R79 | | Resistor, 560,000 ohms, 1 watt | W 00406 05 | 2272 | |
| Resistor, same as R49 Resistor, variable, s00 ohms, 1/2 watt Resistor, R470 ohms, 1/2 watt Resistor, R470 ohms, 1/2 watt Resistor, R470 ohms, 1/2 watt Resistor, same as R3 R71 Resistor, same as R3 R72 Resistor, same as R53 R73 Resistor, same as R54 Resistor, same as R55 R54 Resistor, same as R55 R55 R61 Resistor, same as R55 R61 Resistor, same as R55 R61 Resistor, same as R55 R62 R63 R63 R64 R64 R65 R | | Nesistor, 47 onms, ½ watt | | 3272 3073 | |
| Resistor, same as R19 Resistor, same as R20 Resistor, same as R20 Resistor, same as R30 Resistor, R20,000 ohms, 1 watt. R.90496-52 R.9 | | Resistor, 47,000 onms, I watt | | 7198 | |
| R855 Resistor, 180 ohms, ½ watt K.82283.53 R866 Resistor, variable, 500 ohms C.37829.5 R67 Resistor, 470 ohms, 1 watt K.90496-58 R68 Resistor, 1 megohm, ½ watt K.82283.98 R69 Resistor, same as R19 K.82283.99 R69 Resistor, same as R19 K.82283.99 R71 Resistor, same as R19 K.82283.97 R72 Resistor, same as R19 R.82283.97 R73 Resistor, same as R29 R.82283.97 R74 Resistor, same as R24 R.82283.98 R75 Resistor, same as R2 R.82283.99 R76 Resistor, variable, 50,000 ohms. M.433196-5 R77 Resistor, same as R22 R.803 R80 Resistor, 180,000 ohms, 1 watt K.90496-98 R81 Resistor, 150,000 ohms, 1 watt K.90496-88 R82 Resistor, 2100 ohms, 1 watt K.90496-73 R84 Resistor, wariable, 10,000 ohms M.433196-6 R85 Resistor, wariable, 10,000 ohms M.433196-6 R85 Resi | | Resistor, same as RI | | | |
| Resistor, 470 ohms, 1 watt | 2025 d. | Resistor, 180 ohms, 1/2 watt | *** | | |
| Resistor, 1 megolum, ½ watt. K-90496-58 | | Nesistor, variable, 500 onms | | 3061 | |
| REO REO RESISTOR, 1980,000 ohms, ½ watt. RF0 Resistor, 820,000 ohms, ½ watt. RF1 Resistor, 8283-97 RF1 Resistor, 8283-88 RF2 Resistor, 8283-88 RF3 Resistor, 8283-88 RF3 Resistor, 8283-88 RF3 Resistor, 8283-88 RF4 Resistor, 8284-88 RF5 Resistor, 12 megohms, 1 watt. RF7 Resistor, 12 megohms, 1 watt. RF7 Resistor, 12 megohms, 1 watt. RF7 Resistor, 8283-88 RF7 Resistor, 12 megohms, 1 watt. RF7 Resistor, 8283-88 RF7 Resistor, 150,000 ohms, 1 watt. RF7 Resistor, 8200 ohms, 1 watt. RF2 RF3 RF3 RESISTOR, 150,000 ohms, 1 watt. RF2 RESISTOR, 150,000 ohms, 1 | | Aesistor, 470 onins, r watt | | 5976 3727 | |
| Resistor, same as R3 Resistor, same as R3 Resistor, same as R3 R71 Resistor, same as R3 R72 Resistor, same as R3 R73 Resistor, same as R3 R74 R75 R76 R77 | | Acsistor, I megonin. 1/2 watt | | 3065 | |
| R71 Resistor, same as R19 R72 Resistor, same as R19 R73 Resistor, same as R19 R74 Resistor, same as R54 R75 Resistor, same as R54 R76 Resistor, same as R54 R77 Resistor, same as R2 R77 Resistor, variable, 50,000 ohms, 1 watt R77 Resistor, 12 megohms, 1 watt R78 R89 R89 R89 R89 R89 R89 R89 R89 R89 R8 | | Nesistor, 620,000 onms. ½ watt | | 3016 | |
| R72 Resistor, same as R53 R73 Resistor, same as R54 R74 Resistor, same as R2 R75 Resistor, same as R2 R76 Resistor, same as R2 R776 Resistor, variable, 50,000 ohms, 1 R77 Resistor, 12 megohms, 1 watt R78 Resistor, 12 megohms, 1 watt R79 Resistor, 12 megohms, 1 watt R79 Resistor, same as R36 R81 Resistor, same as R36 R81 Resistor, variable, 10,000 ohms, 1 R82 Resistor, variable, 10,000 ohms, 1 R83 Resistor, variable, 10,000 ohms, 1 R84 Resistor, variable, 10,000 ohms, 1 R85 R86 Resistor, variable, 10,000 ohms R86 R87 Resistor, 1200 ohms, 1 watt R89 R88 R89 Resistor, 1200 ohms, 1 watt R89 R89 Resistor, same as R40 R89 R89 Resistor, same as R40 R89 R89 Resistor, 470 ohms, ½ watt R89 R89 Resistor, 470 ohms, ½ watt R89 R89 Resistor, 22,000 ohms, 1 watt R89 R89 Resistor, 22,000 ohms, 1 watt R89 R89 Resistor, same as R68 R89 R89 R89 Resistor, same as R68 R89 R89 R89 R899 Resistor, same as R68 R89 R89 R89 R899 R89 R89 R89 R89 R89 R89 | | Resistor, same as R3 | | | |
| R73 | | Resistor, same as R53 | | | |
| R75 Resistor, 330,000 ohms, 1 watt R76 Resistor, variable, 50,000 ohms R77 Resistor, 1 megohms, 1 watt R78 Resistor, 1 megohms, 1 watt R78 R89 Resistor, 1 megohms, 1 watt R80 R81 Resistor, 150,000 ohms, 1 watt R81 R82 Resistor, 180,000 ohms, 1 watt R82 R83 Resistor, 180,000 ohms, 1 watt R82 R83 Resistor, variable, 10,000 ohms R83 R84 Resistor, variable, 10,000 ohms R85 | R73 | Resistor, same as R54 | 2 / | = | |
| Resistor, 12 megohms, 1 watt | | Resistor, same as R2 | | | |
| Resistor, 12 megohms, 1 watt | | Resistor, 330,000 ohms, 1 watt | K-90496-92 | 3889 | |
| Resistor, 1 megohm, 1 watt | | vesistor, variable, 50.000 onms | 2000 | 5194 | |
| R80 Resistor, same as R36 Resistor, 150,000 ohms, 1 watt | | Colotti, 1.2 megonins i watt | K-90496-99 | 4301 | |
| R80 Resistor, same as R36 Resistor, 150,000 ohms, 1 watt. Resistor, 150,000 ohms, 1 watt. R82 Resistor, 120,000 ohms, 1 watt. R83 Resistor, 200 ohms, 1 watt. R84 Resistor, 200 ohms, 1 watt. R85 Resistor, 2100 ohms, 1 watt. R86 Resistor, 330,000 ohms, ½ watt. R87 Resistor, 330,000 ohms, ½ watt. R88 R89 Resistor, 15 ohms, ½ watt. R89 Resistor, 15 ohms, ½ watt. R89 Resistor, 15 ohms, ½ watt. R89 Resistor, 470 ohms, ½ watt. R89 Resistor, 470 ohms, ½ watt. R89 Resistor, same as R67 Resistor, 2,000 ohms, 1 watt. R89 Resistor, same as R68 Resistor, 22,000 ohms, ½ watt. R89 Resistor, 22,000 ohms, 1 watt. R89 Resistor, 22,000 ohms, ½ watt. R89 Resistor, 300 ohms, ½ watt. R89 R99 R99 Resistor, 300 ohms, ½ watt. R89 R99 Resistor, 300 ohms, ½ watt. R89 R99 R99 R99 R99 R99 R99 R99 R99 R99 | | Resistor, same as R22 | K-90496-98 | 7199 | |
| R81 Resistor, 150,000 olms, 1 watt R82 Resistor, 180,000 olms, 1 watt R834 Resistor, 8200 olms, 1 watt R84 Resistor, 8200 olms, 1 watt R854 Resistor, 8200 olms, 1 watt R856 Resistor, 1200 olms, 1 watt R856 Resistor, 330,000 olms, 1 watt R857 Resistor, 1200 olms, 1 watt R858 R89 Resistor, 1200 olms, 1 watt R858 R89 Resistor, 1200 olms, 1 watt R858 R89 Resistor, 150 olms, 1 watt R870 Resistor, 150 olms, 1 watt R887 R89 Resistor, 150 olms, 1 watt R888 R89 Resistor, 150 olms, 1 watt R889 Resistor, 150 olms, 1 watt R890 Resistor, 150 olms, 1 watt R891 Resistor, 150 olms, 1 watt R891 Resistor, 150 olms, 1 watt R892 Resistor, 150 olms, 1 watt R893 Resistor, 150 olms, 1 watt R894 Resistor, 220 olms, 1 watt R895 Resistor, 220 olms, 1 watt R896 Resistor, 220 megolms, 1 watt R897 Resistor, 22 megolms, 1 watt R898 R99 Resistor, 22 megolms, 1 watt R898 R99 Resistor, 280 olms, 1 watt R898 R99 Resistor, 3 me as R68 R899 Resistor, 3 me as R68 R890 R90 R90 R90 R90 R90 R90 R90 R90 R90 R | R80 | Resistor, same as R36 | , 102 | | |
| Resistor, variable, 10,000 ohms, 1 watt | | Resistor, 150,000 ohms, 1 watt | K-00406-88 | 3189 | |
| R84 Resistor, 8200 ohms, 1 watt. | | | | 12356 | |
| R85 Resistor, 1200 ohms, 1 watt | | Cololol, Vallable, 10,000 nnms | | 68833 | |
| R87 Resistor, same as R2 Resistor, same as R2 Resistor, same as R88 R89 Resistor, same as R84 Resistor, same as R85 R891 Resistor, same as R85 R892 Resistor, same as R85 R893 Resistor, same as R86 R894 Resistor, same as R86 R894 Resistor, same as R86 R895 Resistor, same as R86 R896 R896 Resistor, same as R86 R897 Resistor, same as R86 R897 Resistor, same as R16 R8101 Resistor, same as R86 R8102 Resistor, same as R86 R8103 Resistor, same as R86 R8104 Resistor, same as R86 R8105 Not Used Resistor, same as R16 R8106 Resistor, same as R16 R8107 Resistor, same as R16 R8108 Resistor, same as R16 R8109 Resistor, same as R57 R8109 Resistor, same as R58 R8101 Resistor, same as R58 R8101 Resistor, same as R56 R8101 Resistor, same as R56 R8101 Resistor, same as R57 R8108 Resistor, same as R57 R8109 Resistor, same as R58 R8101 Resistor, same as R58 R8101 Resistor, same as R50 R8101 | | | | 38888 | |
| R88, R89 | R86 | Resistor, 330,000 ohms. 1/2 watt | | 38896 | |
| Resistor, same as R68 R92 Resistor, same as R68 R94 Resistor, same as R68 R95 Resistor, 22,000 ohms, 1 watt R96 Resistor, 22,000 ohms, 1 watt R97 Resistor, 22,000 ohms, 1 watt R98 R99 Resistor, same as R76 R98 R99 Resistor, 820 ohms, 1/2 watt R100 Resistor, same as R10 R101 Resistor, same as R43 R102 Resistor, same as R43 R102 Resistor, same as R88 R104 Resistor, same as R88 R105 Not Used R106 Resistor, same as R16 R107 Resistor, same as R16 R108 Resistor, same as R16 R109 Resistor, variable, 500,000 ohms R109 Resistor, variable, 500,000 ohms R109 Resistor, same as R68 R109 Resistor, same as R68 R101 Resistor, same as R76 R102 Resistor, same as R76 R103 Resistor, same as R16 R104 Resistor, same as R16 R105 Resistor, same as R16 R107 Resistor, same as R16 R108 Resistor, same as R16 R109 Resistor, same as R8 R100 Resistor, same as R8 R111 R112 Resistor, same as R8 R111 R112 Resistor, same as R8 R111 R112 Resistor, same as R9 R115 Resistor, same as R9 R101 Resistor, same as R103 Resistor, same as R103 Resistor, 300 ohms, 1 watt R119 Resistor, 300 ohms, 1 watt R1100 Resistor, 300 ohms, 2 watts. R1110 Resistor, 300 ohms, 2 watts. R1111 R112 Resistor, 300 ohms, 2 watts. R1121 R121 R121 R121 R121 R121 R121 R12 | | Cololol. Sallic as KZ | K-82283-92 | 14983 | |
| Resistor, same as R68 R94 Resistor, same as R68 R95 Resistor, same as R68 R96 Resistor, 22,000 ohms, 1 watt R97 Resistor, 22,000 ohms, 1 watt R98 Resistor, 22,000 ohms, 1 watt R98 Resistor, 22,000 ohms, 1 watt R99 Resistor, same as R76 R97 Resistor, same as R76 R98 R99 Resistor, same as R10 R99 Resistor, same as R10 R99 Resistor, same as R43 R100 Resistor, same as R43 R101 Resistor, same as R43 R102 Resistor, same as R9 R103 Resistor, same as R58 R104 Resistor, same as R58 R105 Not Used R106 Resistor, same as R16 R107 Resistor, same as R16 R108 Resistor, variable, 500,000 ohms R109 Resistor, 10 ohms, 1 watt R109 Resistor, 10 ohms, 1 watt R111, R112 Resistor, same as R68 R111, R112 Resistor, same as R76 R111 R114 Resistor, same as R76 R116 Resistor, same as R76 R117 Resistor, same as R76 R117 Resistor, same as R76 R118 Resistor, same as R76 R119 Resistor, same as R76 R110 Resistor, same as R76 R111 R112 Resistor, same as R76 R112 Resistor, same as R70 R113 Resistor, same as R76 R116 Resistor, same as R76 R117 Resistor, same as R76 R118 Resistor, 390 ohms, 1 watt R-90496-91 R119 Resistor, 1900 ohms, 1 watt R-90496-91 R110 Resistor, 1900 ohms, 2 watts R111 R112 R112 R112 R112 R114 R114 R114 | | esistor, 15 ohms, ½ watt | K-82283-40 | 11565 | |
| Resistor, same as R68 Resistor, 22,000 ohms, 1 watt Resistor, same as R76 Resistor, same as R68 Rosistor, same as R79 Resistor, same as R79 Rosistor, same as R79 Resistor, same as R16 Resistor, same as R79 Resistor, same as R70 Resistor, sa | | Coloiul, Saille as Kna | 12-02203-10 | 11300 | |
| Resistor, same as R68 Resistor, 22,000 ohms, 1 watt Resistor, 22 megohms, ½ watt Resistor, same as R76 Resistor, same as R68 Resistor, same as R68 Resistor, same as R68 Resistor, same as R68 Resistor, same as R76 Resistor, same as R76 Resistor, same as R76 Resistor, same as R76 Resistor, same as R9 Resistor, same as R9 Resistor, same as R76 Resistor, same as R16 Resistor, same as R16 Resistor, same as R16 Resistor, same as R76 Resistor, same as R77 Resistor, same as R76 Resistor, same as R76 Resistor, same as R77 Resistor, same as R76 Resistor, | | esistor, 4/0 ohms, ½ watt | K-82283-58 | 30499 | |
| Resistor, 22,000 ohms, 1 watt. Resistor, 22 megohms, ½ watt Resistor, same as R76 Resistor, same as R76 Resistor, same as R1 Resistor, same as R68 Resistor, same as R68 Resistor, same as R43 Resistor, same as R43 Resistor, same as R43 Resistor, same as R68 Resistor, same as R76 Resistor, same as R76 Resistor, same as R76 Resistor, same as R16 Resistor, same as R16 Resistor, same as R16 Resistor, variable, 500,000 ohms Resistor | | esister same as D60 | | | |
| Resistor, same as R76 Resistor, same as R76 Resistor, same as R76 Resistor, same as R76 Resistor, same as R68 R101 Resistor, same as R43 Resistor, same as R43 Resistor, same as R9 R102 Resistor, same as R9 R103 Resistor, 470,000 ohms, ½ watt Resistor, same as R16 R106 Resistor, same as R16 Resistor, same as R16 Resistor, variable, 500,000 ohms Resistor, variable, 500,000 ohms Resistor, variable, 500,000 ohms Resistor, same as R68 R111, R112 Resistor, same as R68 Resistor, same as R76 Resistor, same as R94 Resistor, same as R94 Resistor, same as R94 Resistor, same as R94 Resistor, same as R76 Resistor, 47,000 ohms, ½ watt Resistor, 47,000 ohms, ½ watt Resistor, same as R76 Resistor, same as R10 Resistor, same as R94 R | | esistor, 22,000 ohms, 1 watt | TF 00405 70 | #1000 | |
| Resistor, same as R1 Resistor, same as R1 Resistor, same as R68 Resistor, same as R43 Resistor, same as R43 Resistor, same as R9 Resistor, same as R1 Resistor, variable, 500,000 ohms Resistor, variable, 500,000 ohms Resistor, same as R68 Resistor, same as R68 Resistor, same as R68 Resistor, same as R76 Resistor, sam | | Constor, 2.2 megonins. 1/2 warr | | 71989 30649 | |
| Resistor, 820 ohms, ½ watt Resistor, same as R68 Resistor, same as R68 Resistor, same as R9 Resistor, same as R9 Resistor, 470,000 ohms, ½ watt Resistor, same as R16 Resistor, variable, 500,000 ohms Resistor, 10 ohms, 1 watt Resistor, same as R68 Resistor, same as R68 Resistor, same as R76 Resistor, 47,000 ohms, ½ watt Resistor, 47,000 ohms, ½ watt Resistor, 270,000 ohms, 1 watt Resistor, 390 ohms, 2 watts Resistor, 390 ohms, 2 watts Resistor, 100 ohms, 1 waft Resistor, 100 ohms, 1 waft | | conston, same as R/U | K-02203-102 | 30049 | |
| Resistor, same as R43 Resistor, same as R9 Resistor, same as R9 Resistor, same as R58 Not Used Resistor, same as R16 Resistor, same as R16 Resistor, variable, 500,000 ohms. Resistor, variable, 500,000 ohms. Resistor, variable, 500,000 ohms. Resistor, same as R68 Resistor, same as R68 Resistor, same as R77 Resistor, same as R94 Resistor, same as R94 Resistor, same as R76 Resistor, same as R103 Resistor, 390 ohms, 1 watt Resistor, 100 ohms, 1 watt Resistor, 100 ohms, 1 watt Resistor, 100 ohms, 1 watt | | esistor, same as R1 | 2 2 2 2 | | |
| R101 Resistor, same as R43 Resistor, same as R9 Resistor, 470,000 ohms, ½ watt Resistor, same as R58 Not Used Resistor, same as R16 Resistor, same as R16 Resistor, same as R1 Resistor, variable, 500,000 ohms Resistor, 10 ohms, 1 watt Resistor, same as R68 Resistor, same as R68 Resistor, same as R57 Resistor, same as R57 Resistor, same as R94 Resistor, same as R94 Resistor, same as R76 Resistor, same as R76 Resistor, same as R76 Resistor, same as R76 Resistor, 47,000 ohms, ½ watt Resistor, 270,000 ohms, 1 watt Resistor, same as R103 Resistor, 390 ohms, 2 watts Resistor, 100 ohms, 1 waft | | esistor, 820 onms, ½ watt | K-82283-61 | 30158 | |
| Resistor, same as R9 Resistor, 470,000 ohms, ½ watt Resistor, same as R58 Not Used Resistor, same as R16 Resistor, same as R16 Resistor, variable, 500,000 ohms Resistor, same as R68 Resistor, same as R68 Resistor, same as R68 Resistor, same as R76 Resistor, same as R103 Resistor, 100 ohms, ½ watt | | | K | * × = , = | |
| Resistor, 470,000 ohms, ½ watt Resistor, same as R58 Not Used Resistor, same as R16 Resistor, same as R1 Resistor, variable, 500,000 ohms Resistor, variable, 500,000 ohms Resistor, same as R68 Resistor, same as R68 Resistor, same as R77 Resistor, same as R77 Resistor, same as R94 Resistor, same as R94 Resistor, same as R76 Resistor, same as R76 Resistor, same as R76 Resistor, same as R76 Resistor, 47,000 ohms, ½ watt Resistor, variable, 500,000 ohms Resistor, same as R68 Resistor, same as R68 Resistor, same as R77 Resistor, same as R76 Resistor, same as R76 Resistor, 47,000 ohms, ½ watt Resistor, 500 ohms, ½ watt Resistor, 500 ohms, ½ watt Resistor, 500 ohms, ½ watt Resistor, 100 ohms, ½ watt Resistor, 100 ohms, ½ watt Resistor, 100 ohms, ½ watt | | esistor same as DO | 0 \(\frac{1}{2}\) \(\text{A}\) | | |
| Not Used Resistor, same as R16 Resistor, same as R16 Resistor, variable, 500,000 ohms Resistor, 47,000 ohms, 1 watt Resistor, 500,000 ohms, 1 watt Resistor, 500,000 ohms, 1 watt Resistor, 500,000 ohms, 1 watt Resistor, 390 ohms, 2 watts Resistor, 100 ohms, 1 watt Resistor, 500,000 ohms, 1 watt Resistor, 100 ohms, 1 watt Resistor, 500,000 ohms, 2 watts Resistor, 100 ohms, 1 watt Resistor, 500,000 ohms, 2 watts Resistor, 100 ohms, 1 watt Resistor, 100 ohms, 1 watt Resistor, 500,000 ohms, 2 watts Resistor, 100 ohms, 1 watt Resistor, 500,000 ohms, 2 watts Resistor, 100 ohms, 1 watt Resistor, 500,000 ohms, 2 watts Resistor, 100 ohms, 1 watt Resistor, 500,000 ohms, 2 watts Resistor, 5 | | esistor, 470,000 ohms, ½ watt | IZ 92293 04 | 20649 | |
| Resistor, same as R16 Resistor, variable, 500,000 ohms Resistor, variable, 500,000 ohms Resistor, 10 ohms, 1 watt Resistor, same as R68 Resistor, same as R68 Resistor, same as R77 Resistor, same as R77 Resistor, same as R94 Resistor, same as R76 Resistor, variable, 500,000 ohms Resistor, same as R68 Resistor, same as R76 Resistor, same as R76 Resistor, same as R76 Resistor, 47,000 ohms, ½ watt Resistor, 270,000 ohms, 1 watt Resistor, same as R103 Resistor, 390 ohms, 2 watts Resistor, 100 ohms, 1 watt Resistor, 100 ohms, 1 watt | | esistor, same as Roo | 11-02203-94 | 30648 | |
| Resistor, same as R1 Resistor, variable, 500,000 ohms. Resistor, 10 ohms, 1 watt. Resistor, same as R68 Resistor, same as R57 Resistor, same as R76 Resistor, 47,000 ohms, ½ watt. Resistor, 270,000 ohms, 1 watt. Resistor, same as R103 Resistor, 390 ohms, 2 watts Resistor, 100 ohms, 1 watt Resistor, 100 ohms, 1 watt Resistor, 100 ohms, 1 watt | | | a a Million | | |
| Resistor, variable, 500,000 ohms Resistor, 10 ohms, 1 watt Resistor, same as R68 Resistor, same as R57 Resistor, same as R77 Resistor, same as R94 Resistor, same as R94 Resistor, same as R76 Resistor, same as R76 Resistor, same as R76 Resistor, same as R76 Resistor, ame as R76 Resistor, ame as R76 Resistor, 270,000 ohms, ½ watt Resistor, 270,000 ohms, 1 watt Resistor, same as R103 Resistor, 390 ohms, 2 watts Resistor, 100 ohms, 1 watt Resistor, 100 ohms, 1 watt | | | 2 89 | | |
| Resistor, 10 ohms, 1 watt Resistor, same as R68 Resistor, same as R57 Resistor, same as R57 Resistor, same as R94 Resistor, same as R94 Resistor, same as R76 Resistor, same as R76 Resistor, same as R76 Resistor, 47,000 ohms, ½ watt Resistor, 270,000 ohms, 1 watt Resistor, same as R103 Resistor, 390 ohms, 2 watts Resistor, 100 ohms, 1 watt Resistor, 100 ohms, 1 | | esistor, variable 500 000 ohms | | | |
| Resistor, same as Ros Resistor, same as Ros Resistor, same as R57 Resistor, same as R2 Resistor, same as R94 Resistor, same as R5 Resistor, same as R5 Resistor, same as R76 Resistor, 47,000 ohms, ½ watt Resistor, 270,000 ohms, 1 watt Resistor, same as R103 Resistor, 390 ohms, 2 watts Resistor, 100 ohms, 1 watt Resistor, 100 ohms, 1 wa | | esistor, 10 onms, 1 watt | | 52444 | |
| 113 Resistor, same as R2 114 Resistor, same as R94 115 Resistor, same as R94 116 Resistor, same as R76 117 Resistor, 47,000 ohms, ½ watt 118 Resistor, 270,000 ohms, 1 watt 119 Resistor, same as R103 120 Resistor, 390 ohms, 2 watts 121 Resistor, 100 ohms, 1 watt 15 Resistor, 100 ohms, 1 watt 16 Resistor, 100 ohms, 2 watts 17 Resistor, 100 ohms, 1 watt | | esistor, same as Ros | K-90496-38 | 69640 | |
| 114 Resistor, same as R94 115 Resistor, same as R5 116 Resistor, same as R76 117 Resistor, 47,000 ohms, ½ watt 118 Resistor, 270,000 ohms, 1 watt 119 Resistor, same as R103 120 Resistor, 390 ohms, 2 watts 121 Resistor, 100 ohms, 1 watt 121 Resistor, 100 ohms, 1 watt | | esistor, same as R57 | | | |
| 115 Resistor, same as R5 116 Resistor, same as R76 117 Resistor, 47,000 ohms, ½ watt 118 Resistor, 270,000 ohms, 1 watt 119 Resistor, same as R103 120 Resistor, 390 ohms, 2 watts 121 Resistor, 100 ohms, 1 watt 15 Resistor, 100 ohms, 1 watt 16 Resistor, 100 ohms, 2 watts 17 Resistor, 100 ohms, 1 watt | | | | | |
| 116 Resistor, same as R76 117 Resistor, 47,000 ohms, ½ watt 118 Resistor, 270,000 ohms, 1 watt 119 Resistor, same as R103 120 Resistor, 390 ohms, 2 watts 121 Resistor, 100 ohms, 1 watt 15 Resistor, 100 ohms, 1 watt 16 Resistor, 270,000 ohms, 1 watt 17 Resistor, 390 ohms, 2 watts 18 Resistor, 100 ohms, 1 watt 19 Resistor, 100 ohms, 1 watt | | existor, same as K94 | E | | |
| 117 Resistor, 47,000 ohms, ½ watt 118 Resistor, 270,000 ohms, 1 watt 119 Resistor, same as R103 120 Resistor, 390 ohms, 2 watts 121 Resistor, 100 ohms, 1 watt Resistor, 100 ohms, 1 watt | 116 | esistor, same as R76 | * 1 | | |
| Resistor, 270,000 ohms, 1 watt. Resistor, same as R103 Resistor, 390 ohms, 2 watts. Resistor, 100 ohms, 1 watt K-90496-91 K-90496-91 K-99126-57 Sesistor, 100 ohms, 1 watt | 117 | esistor, 47,000 ohms 1/2 watt | 77 00000 | | |
| 120 Resistor, 390 ohms, 2 watts. 121 Resistor, 100 ohms, 1 watt | | esistor, 270,000 onms. I watt | | 30787 | |
| Trocator, 100 Ulling, I warr | | | K-90490-91 | 19232 | |
| Traction, 100 Ulling, I watt | | esistor, 390 ohms, 2 watts | K-99126-57 | 51212 | |
| | | corotor, 100 dillis, I warr | | 31212 | |
| Incorptor, 0000 thins. I warr | | esistor, dood onins, I watt | | 38887 | |
| Resistor, same as Roz | | sistor, same as Roz | | | |
| Resistor, same as R103 | | esistor, same as R3 | No. 1 | | |

| SYMBOL No. | DESCRIPTION | DRAWING No. | STOCK No. |
|---------------|--|--|--------------|
| R126 | Resistor, variable, 2.5 megohms | M-427471-33 | 54159 |
| R127 | Resistor, variable, 2000 ohms | M-433196-17 | 52011 |
| R128 | Resistor, same as R3 | The second secon | A STREET OF |
| R129 | Resistor, 2200 ohms, 1 watt | K-90496-66 | 71991 |
| R130, R131 | Resistor, variable, 20 ohms | M-433196-37 | 54416 |
| S1 | Switch, DPDT | M-95559-5 | 93263 |
| S2A | Switch, interlock | K-99119-1 | 54591 |
| S2B | Plug, interlock switch | K-99119-2 | 54592 |
| T1 | Transformer, power | M-901918-2 | 59763 |
| T2 | Transformer, vertical output | K-895383-1 | 51910 |
| T3 | Transformer, horizontal output | M-901813-1 | 51911 |
| X1 to X18 | Socket | K-99390-1 | 54414 |
| X19 | Socket | K-837884-2 | 43163 |
| X20 | Socket | K-856956-9 | 54160 |
| Y1, Y2 | Crystal, 1N48 | | 54374 |
| XF1 | Socket, fuse | K-99088-1 | 58933 |
| = | MISCELLANEOUS | 1 | |
| | Mounting plate, steel, for capacitor C6 | K-85559-2 | . a |
| | Mounting plate, steel, for capacitors C2, C3, C7, C10, C22 | K-85559-3 | |
| | Mounting plate, phenolic, for capacitors C18, C24 | K-85558-2 | 28452 |
| 1 | Shield Assembly, monoscope | T-618751-501 | 51989 |
| | Knob, for R36, R76, R80, R83, R96, R116, R130 R131 | P-712336-507 | 30075 |
| | Termination, coaxial | K-895438-501 | 54256 |

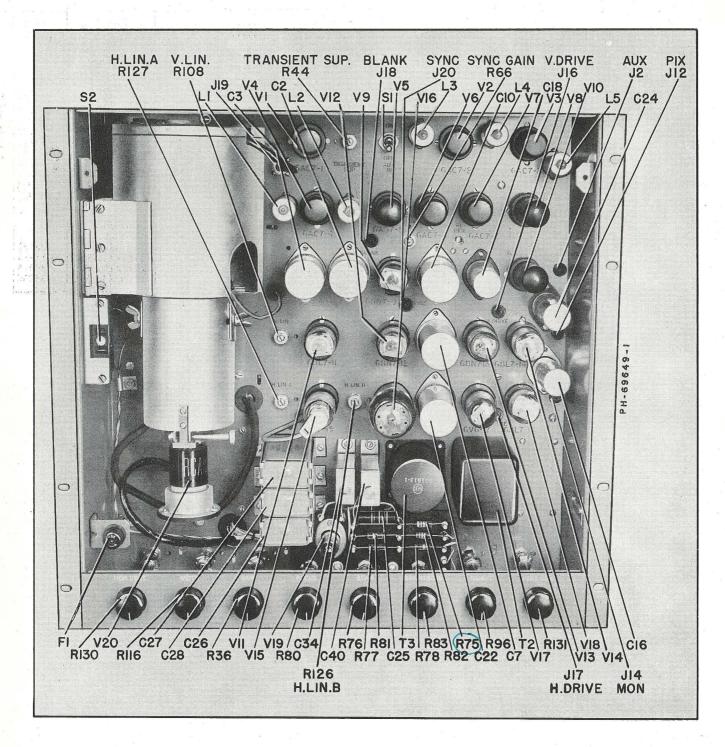


Figure 5-Monoscope Camera, Front View

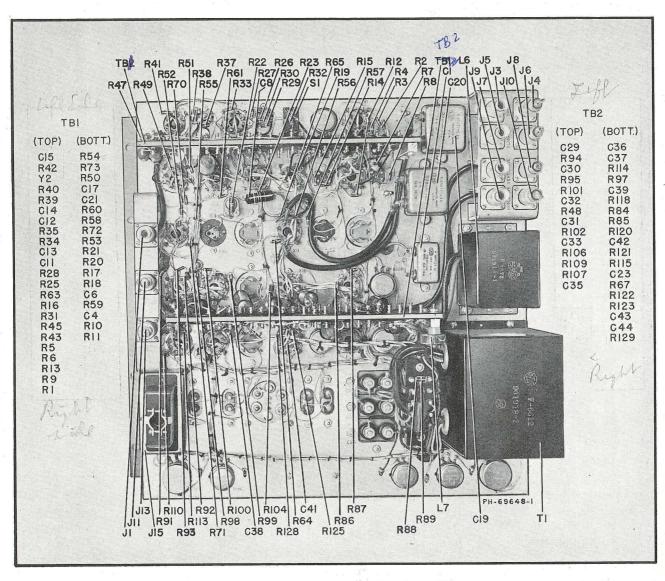


Figure 6-Monoscope Camera, Rear View


TK-1B MONOSCOPE CAMERA

| TUBE | | | GRID | | | | | PLATE | | | | C | SCREEN | | | |
|--------|-------------------|----------------------|--------------|------|-------------|--|-----|-------|------|--|------|-------|-------------|--------------------|------|---------|
| SYMBOL | RCA TYPE | FUNCTION | PIN | VOI | TAGE AC* | | PIN | VOI | TAG | | PIN | VOL | TAGE AC* | | PIN | VOLTAG |
| V1 | 6AC7 | VIDEO AMP. | 4 | 0 | 1 | | 8 | 168 | | | 5 | 1.7 | 1 | | 6 | 163 |
| V2 | 6AC7 | VIDEO AMP. | 4 | 0 | 1.0 | J. J | 8 | 275 | 9.6 | JANANA WANA WANA WANA WANA WANA WANA WAN | 5 | 2.2 | | -: | 6 | 155 |
| V3 | 6AC7 | VIDEO AMP. | 4 | -2.5 | 9.6 | MWWWWW. | 8 | 160 | 6.3 | Twwwww. | 5 | 1.25 | 2.0 | MANAMANA | 6 | 160 |
| V4 | 6AC7 | VIDEO AMP. | 4 | 0 | | | 8 | 268 | | , pariting | 5 | 2 | | | 6 | 165 |
| V5 | 6AG7 | VIDEO AMP. | 4 | 0 | 3.0 | ~~~ | 8 | 270 | 5.0 | [] | 5 | 2.9 | 3.0 | "WWWWWWW"" | 6 | 152 |
| V6 | 6AC7 | VIDEO AMP. | 4 | 0 | | | 8 | 220 | 1.0 | SAME AS GRID V2 | 5 | 1.9 | 0 | | 6 | 145 |
| V7 | 6AC7 | BLANKING AMP. | 4 | -2.4 | 7.0 | П | 8 | 275 | 9.6 | Milmilliam | 5 | 0.15 | 0.7 | пп | 6 | 70 |
| V8 | 6AG7 | VIDEO OUTPUT | 4 | 0 | 5.5 | [] | 8 | 200 | 2.0 | []HAMMAMAMA(] | 5 | 2.9 | 3.2 | Twwwww. | 6 | 160 |
| V9A | 1/2 6SN7 | SYNC. AMP. | 1 | 0 | 4.7 | | 2 | 281 | 2.3 | | 3 | 1.1 | 3.0 | | - | - |
| V9B | 1/2 6SN7 | BLANKING AMP. | 4 | -1.1 | 3.5 | | 5 | 208 | 7.0 | П | 6 | 0.03 | 0.08 | | - | |
| V10 | 6AG7 | VIDEO OUTPUT | 4 | 0 | 5.5 | SAME AS V8 | 8 | 200 | 2.0 | SAME AS V8 | 5 | 2.8 | 3.2 | SAME AS V8 | 6 | 160 |
| V11A | 1/2 6SL7 | VERT. FEEDBACK AMP. | 1 | -1.4 | 0, 08 | HHHHHHHHH | 2 | 189 | 2.9 | Immunitarian Indian | 3 | -0.8 | 0.65 | THIHHHHHHHHH | - | - |
| V11B | 1/2 6SL7 | REGULATOR, H. V. | 4 | -0.6 | 0.1 | | 5 | 95 | 8.0 | | 6 | 0 | 0 | | _ | 1 |
| V12A | 1/2 6SN7 | VERT. OUTPUT | 1 | 0 | 18 | | 2 | 268 | 85 | TT | 3 | 9 | 10 | 1 | - | - |
| V12B | 1/2 6SN7 | SYNC. AMP. | 4 | 155 | 2.9 | | 5 | 285 | 0 | | 6 | 165 | 5- | Tunamanana T | | - |
| V13A | 1/2 6SN7 | 1st VERT. S. T. AMP. | 1 | 0.05 | 1.4 | | 2 | 189 | 2.9 | | 3 | 5 | 1, 2 | | _ | - |
| V13B | 1/2 6SN7 | 2nd VERT. S. T. AMP. | 4 | 0 | 2,9 | | 5 | 209 | 17.5 | | 6 | 5.9 | 1.3 | | - | |
| 714A | 1/2 6SL7 | VERT. DRIVE AMP. | 1 | 0 | 4,0 | | 2 | 138 | 30 | 11 | 3 | 4.2 | 1.3 | 1 | - | - |
| 714B | 1/2 6SL7 | VERT. DISCHARGE | 4 | -26 | 30 | 11 | 5 | 0.1 | 1.4 | | 6 | 0 | | 1 | - | - |
| 715 | 1B3GT | H. V. RECTIFIER | - | - | | c | AP | 1250 | | | 2,7 | 95 | 8.0 | HAHAMAKAHAMAKAHAMA | - | - |
| 716 | 6Y6G | HOR. DAMPER | 5 | -72 | 520 | TV | 3 | -3.3 | 720 | VV | 8 | 6 | 1.2 | YY | 4 | -3.3 |
| 717 | 6V6GT | HOR. OUTPUT | 5 | 0 | 18 | | 3 | 282 | 880 | √ | 8 | 17 | 0.9 | | 4 | 285 |
| 718A | 1/2 6SL7 | HOR. DRIVE AMP. | 1 | -1 | 3.8 | | 2 | 145 | 30 | \prod | 3 | 0.05 | 0.09 | U U | - | - |
| 718B | 1/2 6SL7 | HOR. DISCHARGE | 4 | -26 | 30 | \\ | 5 | 167 | 18 | V-V | 6 | 0. 02 | | | - | - |
| 19 | 991 | REGULATOR | - | - | 12 | | - | 1190 | | | - | 1140 | | | - | - |
| | | | 8 | | 3 | 41 | | 100 m | | | | | | | , | |
| 1100 | 97704 | | PIN : | NO. | | 1 2 | 17 | 3 | | 5 | 6 | T | 7 | 8 COI | LLEC | TOR CAP |
| V20 | 20 2F21 MONOSCOPE | | DC VOLTAGE - | | | - 0 | - | -600 | | -800 | -800 | 0 | - / , | - 2 | 280 | |

Approximate normal output conditions simulated, 75-ohm terminations used. All dc voltages measured to ground, with RCA VoltOhmyst, Jr. Voltages used: filament 6.3 v. ac; line 115 v. ac; power supply 280 v. dc and -3 v. dc.

Figure 7-Voltage and Waveform Chart

^{*}Peak to peak, 60 cycle sweep.

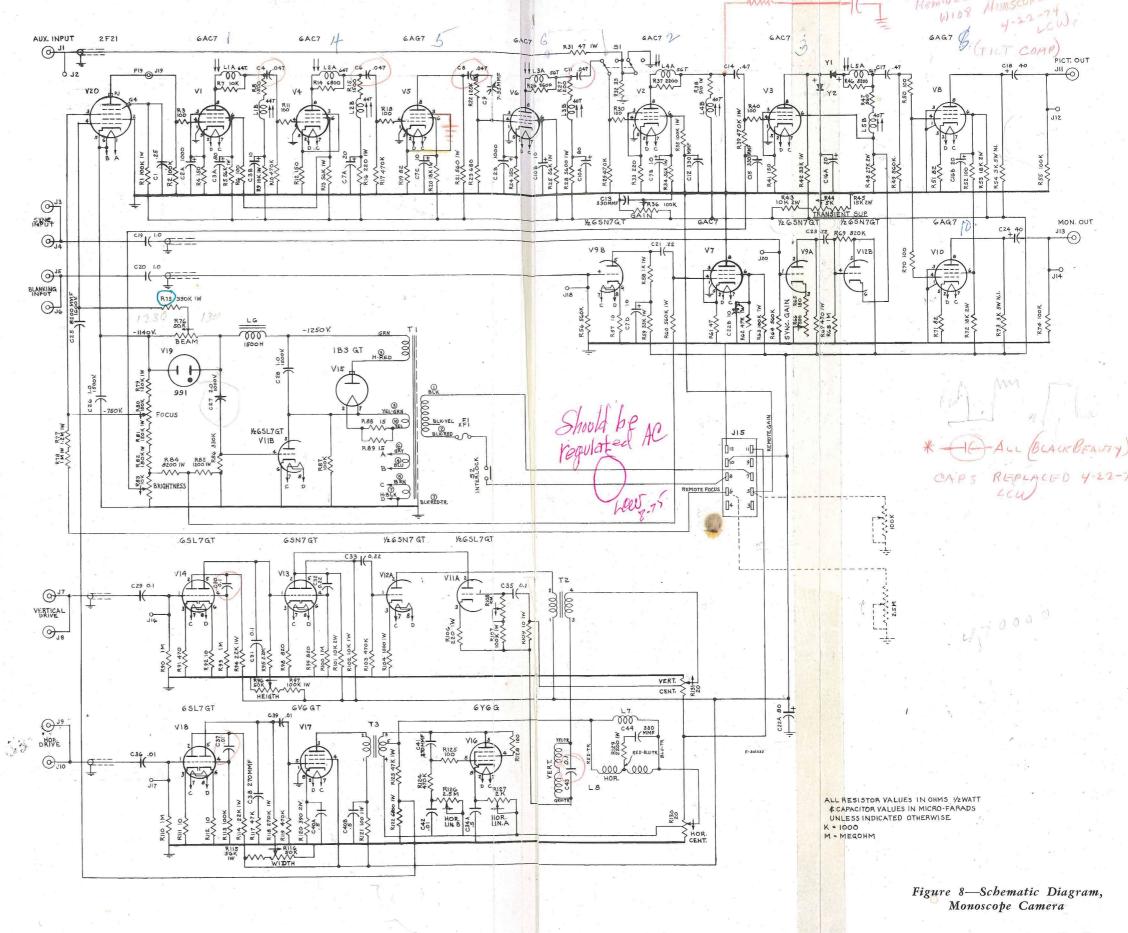

22K



RADIO CORPORATION OF AMERICA ENGINEERING PRODUCTS DEPARTMENT CAMDEN, N. J.